

VHDL Code Simulation & Implementation in ISE Xilinx

vending_machine_processor:

contains: accumulator8, Adder8, full_Adder,
comparator8, comparator_1bit, comparator_co,
mux21, subtractor8

Mohammad Niknam

Reference:

https://github.com/MohammadNiknam17/vending_machine_processor

Block Diagram:

 


Figure 1

Project Description:

Basic 8-bit vending machine processor design which offers support for two drinks and currency of 5 cent, 10 cent, 25 cent denominations.

As an engineer working in a high tech company, asked to implement a RTL description of a vending machine processor using VHDL to control a vending machine.

Figure 1 shows the block diagram of the vending machine.

Here is how the vending machine is supposed to work:

The machine has a single coin slot that accepts nickels, dimes and quarters, one at a time. A coin sensor provides the processor with a 1-bit input C that becomes 1 when a coin is detected, and an 8-bit input V indicating the coin's value in cents. Two 8-bit inputs SO and S1 indicate the cost of the two types of soda drink. Note that the value of SO and S1 can be set by the vending machine owner. Choice is a 1-bit input to the vending machine indicating the type of soda drink selected (Choice 0 is for soda drink type 0 with the cost SO and Choice 1 is for soda drink type 1 with cost of S1).

If the amount of money deposited is less than the cost of the soda, the processor generates an 8-bit output P to display the amount of money deposited in cents. Once the processor has seen coins whose value equals or exceeds the cost of a soda, the processor should set an 2-bit output D for one clock cycle, causing a soda to be dispensed (00 or 11 for no action, 01 for the release of soft drink type 0, and 10 for the release of soft drink type 1).

The vending machine also should generate the 8-bit output E indicating the change to be returned in cents.

Question Link:

<https://www.chegg.com/homework-help/questions-and-answers/junior-engineer-working-high-tech-company-asked-implement-rtl-description-vending-machine--q36105103>

vending_machine:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name: vending_machine_processor
3  -- Module Name: vending_machine - rtl
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity vending_machine is
9      port(
10         nRST : in std_logic; --negative reset
11         clk : in std_logic;
12         C : in std_logic; --from coin sensor: becomes 1 when a coin is detected.
13         V : in std_logic_vector(7 downto 0); --received coin's value in cents from
            coin sensor.
14         S0 : in std_logic_vector(7 downto 0); --price of choice 0, defined by
            vending machin owner.
15         S1 : in std_logic_vector(7 downto 0); --price of choice 1, defined by
            vending machin owner.
16         choice : in std_logic;
17         P : out std_logic_vector(7 downto 0); --Display
18         E : out std_logic_vector(7 downto 0); --return change
19         D : out std_logic_vector(1 downto 0) --soda dispensation
20     );
21 end vending_machine;
22
23 architecture rtl of vending_machine is
24     component accumulator8 is
25         port(
26             clk: in std_logic;
27             nRST_acc: in std_logic;
28             C : in std_logic; --becomes 1 when a coin is detected.
29             data_in : in std_logic_vector(7 downto 0);
30             data_out : out std_logic_vector(7 downto 0)
31         );
32     end component;
33
34     component subtractor8 is
35         port(
36             a : in std_logic_vector(7 downto 0);
37             b : in std_logic_vector(7 downto 0);
38             result : out std_logic_vector(7 downto 0)
39         );
40     end component;
41
42     component comparator8 is
43         port(
44             a : in std_logic_vector(7 downto 0);
45             b : in std_logic_vector(7 downto 0);
46             g_out : out std_logic;
47             e_out : out std_logic;
48             l_out : out std_logic);
49     end component;
50
51     component mux21 is
52         port(
53             A : in std_logic_vector(7 downto 0);
54             B : in std_logic_vector(7 downto 0);
55             s : in std_logic;
56             output : out std_logic_vector(7 downto 0)
57         );
58     end component;
59
60     type FSMTYPE is (INIT_STATE, Coin_Reception, soda_dispensation);
61
62     signal CSTATE, NSTATE : FSMTYPE;
63     signal balance, price, price_reg, coins_to_return : std_logic_vector(7 downto 0);
64     signal price_choice_reg_EN, balance_greater, balance_equal, balance_lower: std_logic;
65     signal choice_reg, dispensation_EN : std_logic;
66     signal nRST_acc : std_logic;
```

vending_machine:

```
71  begin
72      price_registration : process( CLK )
73      begin
74          if (CLK'event and CLK = '1') then
75              if (price_choice_reg_EN = '1') then
76                  price_reg <= price;
77                  choice_reg <= choice;
78              end if ;
79          end if ;
80      end process ; -- price_registration
81
82
83      state_registration : process( CLK )
84      begin
85          if (CLK'event and CLK = '1') then
86              if (nRST = '0') then
87                  CSTATE <= INIT_STATE;
88              else
89                  CSTATE <= NSTATE;
90              end if ;
91          end if ;
92      end process ; -- state_registration
93
94      soda_dispensation_proc: process(clk)
95      begin
96          if (CLK'event and CLK = '1') then
97              if (dispensation_EN = '1') then
98                  if(choice_reg = '0') then
99                      D <= "01"; --S0
100                 else
101                     D <= "10"; --S1
102                 end if;
103             else
104                 D <= "00";
105             end if;
106         end if;
107     end process; --soda_dispensation_Proc;
108
109     next_state : process( CSTATE, balance, C, balance_equal, balance_greater,
110                           coins_to_return)
111     begin
112         NSTATE <= CSTATE;
113         nRST_acc <= '1';
114         price_choice_reg_EN <= '0';
115         dispensation_EN <= '0';
116         p <= (others => '0');
117         E <= (others => '0');
118
119         case( CSTATE ) is
120             when INIT_STATE =>
121                 nRST_acc <= '0';
122                 price_choice_reg_EN <= '1';
123                 E <= balance;
124                 if (C = '1') then
125                     nRST_acc <= '1';
126                     NSTATE <= Coin_Reception;
127                 end if ;
128
129             when Coin_Reception =>
130                 P <= balance;
131                 if (balance_equal = '1' or balance_greater = '1') then
132                     NSTATE <= soda_dispensation ;
133                 end if ;
134
135             when soda_dispensation =>
136                 dispensation_EN <= '1';
137                 E <= coins_to_return;
138                 nRST_acc <= '0';
139                 NSTATE <= INIT_STATE;
140
141             when others =>
142                 end case ;
143         end process ; -- next_state
```

vending_machine:

```
147     mux : mux21 port map(S0, S1, choice, price);
148     accumulator : accumulator8 port map (clk, nRST_acc, C, V, balance);
149     comparator : comparator8 port map (balance, price_reg, balance_greater,
150     balance_equal, balance_lower);
151     subtractor : subtractor8 port map (balance, price_reg, coins_to_return);
152 end rtl;
153
154
```


vending_machine_TB:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name: vending_machine_processor
3  -- Module Name: vending_machine_TB
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  ENTITY vending_machine_TB IS
9  END vending_machine_TB;
10
11 ARCHITECTURE behavior OF vending_machine_TB IS
12     -- Component Declaration for the Unit Under Test (UUT)
13
14     COMPONENT vending_machine
15     PORT(
16         nRST : IN  std_logic;
17         clk  : IN  std_logic;
18         C    : IN  std_logic;
19         V    : IN  std_logic_vector(7 downto 0);
20         S0   : IN  std_logic_vector(7 downto 0);
21         S1   : IN  std_logic_vector(7 downto 0);
22         choice : IN  std_logic;
23         P    : OUT std_logic_vector(7 downto 0);
24         E    : OUT std_logic_vector(7 downto 0);
25         D    : OUT std_logic_vector(1 downto 0)
26     );
27     END COMPONENT;
28
29     --Inputs
30     signal nRST : std_logic := '0';
31     signal clk  : std_logic := '0';
32     signal C    : std_logic := '0';
33     signal V    : std_logic_vector(7 downto 0) := (others => '0');
34     signal S0   : std_logic_vector(7 downto 0) := (others => '0');
35     signal S1   : std_logic_vector(7 downto 0) := (others => '0');
36     signal choice : std_logic := '0';
37
38     --Outputs
39     signal P : std_logic_vector(7 downto 0);
40     signal E : std_logic_vector(7 downto 0);
41     signal D : std_logic_vector(1 downto 0);
42
43     -- Clock period definitions
44     constant clk_period : time := 10 ns;
45
46     constant S0price : std_logic_vector(7 downto 0) := "00100001"; --soda S0 price=
47     33 cent
48     constant S1price : std_logic_vector(7 downto 0) := "01000001"; --soda S1 price=
49     65 cent
50
51     constant Nickel : std_logic_vector(7 downto 0) := "00000101"; --us_coin value= 5
52     cent
53     constant Dime : std_logic_vector(7 downto 0) := "00001010"; --us_coin value= 10
54     cent
55     constant Quarter : std_logic_vector(7 downto 0) := "00011001"; --us_coin value=
56     25 cent
57
58 BEGIN
59     -- Instantiate the Unit Under Test (UUT)
60     uut: vending_machine PORT MAP (
61         nRST => nRST,
62         clk  => clk,
63         C    => C,
64         V    => V,
65         S0   => S0,
66         S1   => S1,
67         choice => choice,
68         P    => P,
69         E    => E,
70         D    => D
71     );
```

vending_machine_TB:


```
77     CLK <= not(CLK) after clk_period/2;
78     nRST <= '0', '1' after 150 ns; -- hold reset state for 400 ns.
79     s0 <= S0price; --soda S0 price= 33 cent
80     S1 <= S1price; --soda S1 price= 65 cent
81     choice <= '1', '0' after 500 ns;
82     C <= '0', '1' after 300 ns, '0' after 310 ns, '1' after 350ns, '0' after 360 ns,
83         '1' after 400 ns, '0' after 410 ns, '1' after 450ns, '0' after 460 ns,
84         '1' after 600 ns, '0' after 610 ns, '1' after 650ns, '0' after 660 ns,
85         '1' after 700 ns, '0' after 710 ns;
86
87     v <= (others => '0'), Quarter after 290 ns, Nickel after 340 ns, Dime after 400
88         ns, Quarter after 440 ns,
89     Quarter after 600 ns, Nickel after 650 ns, Dime after 700 ns, (others => '0')
90     after 710 ns;
91
92 END;
```


vending_machine Simulation:

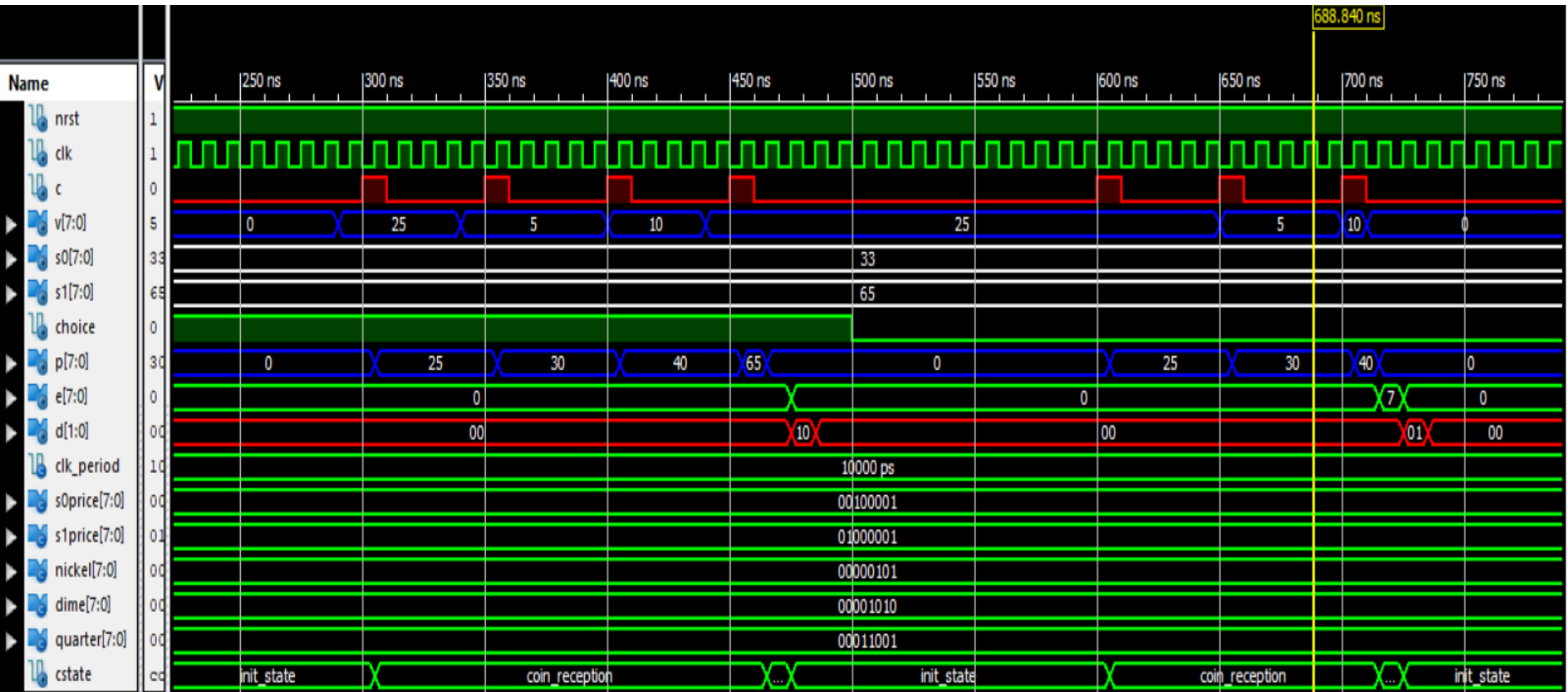


vending_machine Synthesize & RTL Schematic:

vending_machine

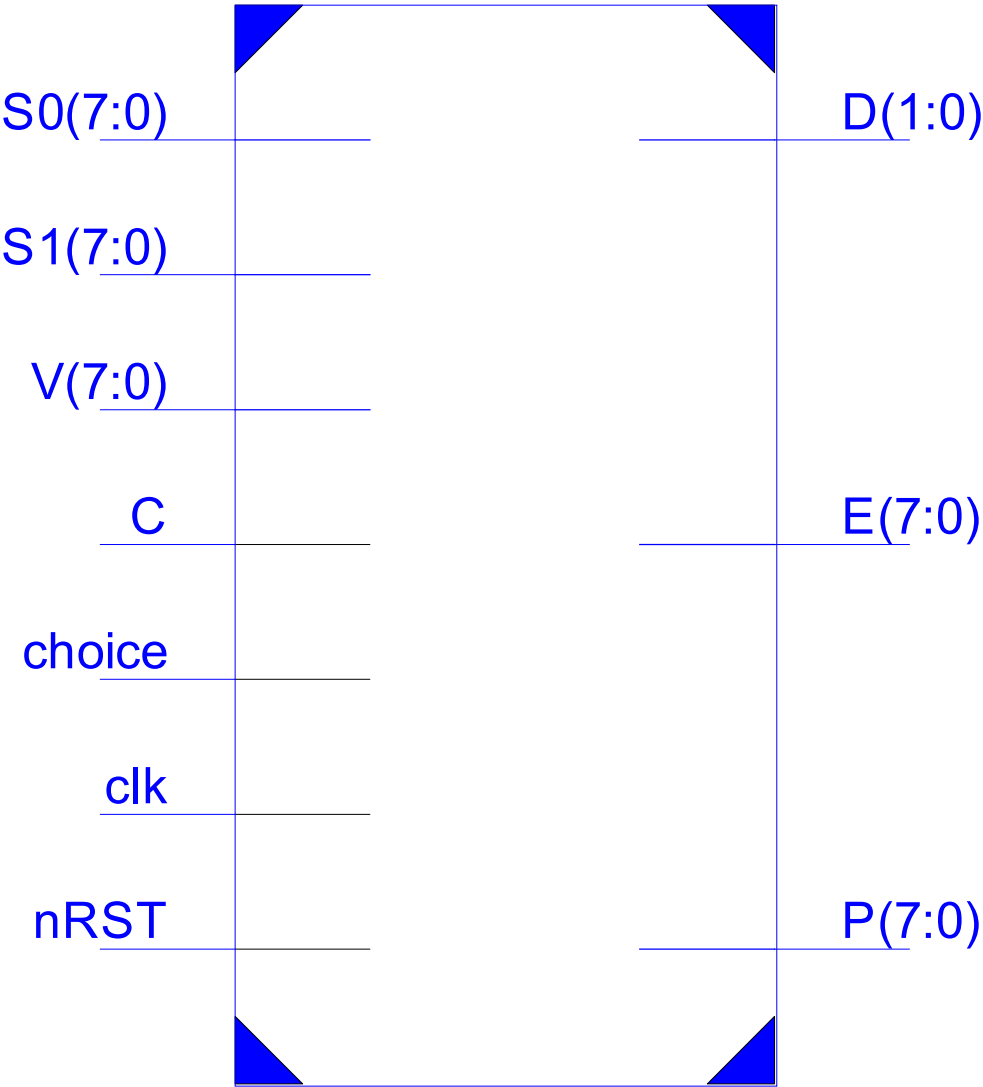


vending_machine

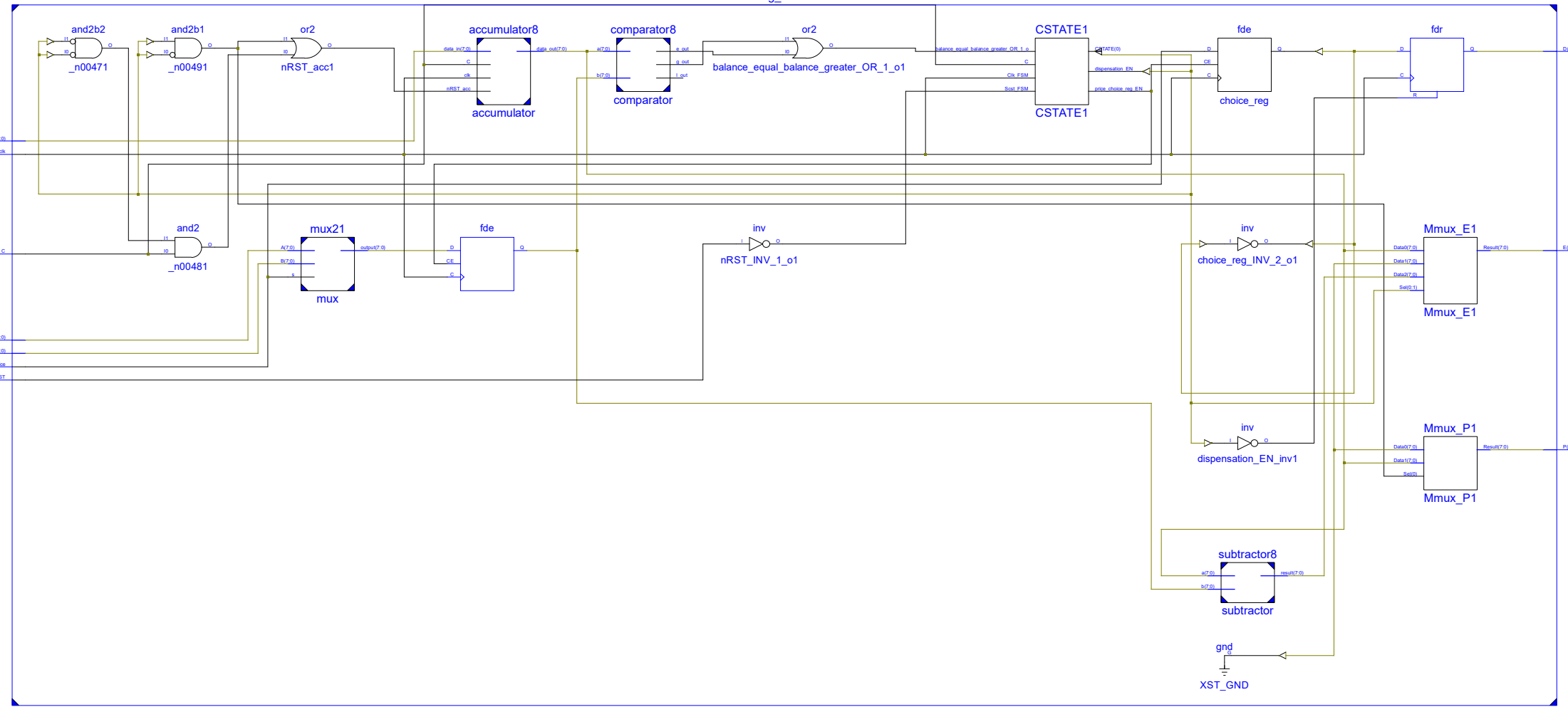vending_machine Synthesize & RTL Schematic:



vending_machine Synthesize & RTL Schematic:

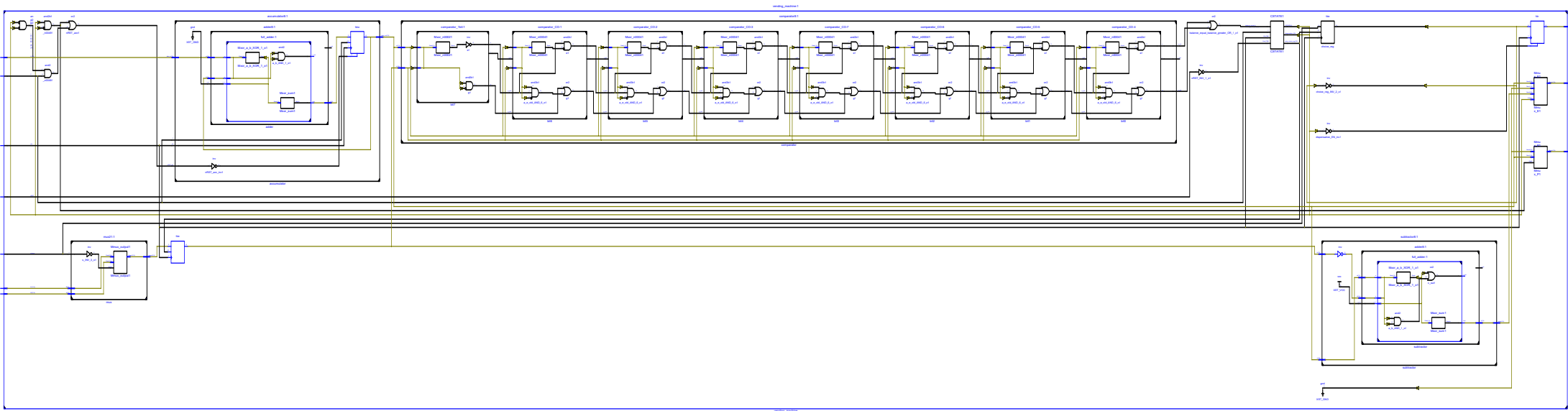


accumulator8:

VHDL CODE


```
1  -- Engineer: Mohammad Niknam
2  -- Project Name: vending_machine_processor
3  -- Module Name: accumulator8
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity accumulator8 is
9      port(
10         clk : in std_logic;
11         nRST_acc : in std_logic;
12         C : in std_logic; --becomes 1 when a coin is detected.
13         data_in : in std_logic_vector(7 downto 0);
14         data_out : out std_logic_vector(7 downto 0)
15     );
16 end accumulator8;
17
18 architecture rtl of accumulator8 is
19     component adder8 IS
20         port(
21             a : in std_logic_vector(7 downto 0);
22             b : in std_logic_vector(7 downto 0);
23             c_in: in std_logic;
24             s: out std_logic_vector(7 downto 0);
25             c_out: out std_logic
26         );
27     end component;
28
29     signal temp1 : std_logic_vector(7 downto 0);
30     signal temp2 : std_logic_vector(7 downto 0);
31     signal c_in : std_logic;
32     signal c_out : std_logic;
33
34     begin
35         c_in <= '0';
36
37         adder : adder8 port map (data_in, temp2, c_in, temp1, c_out);
38
39         reg: process(clk)
40         begin
41             if (clk'event and clk = '1') then
42                 if nRST_acc = '0' then
43                     temp2 <= (others => '0');
44                 elsif (C = '1') then
45                     temp2 <= temp1;
46                 end if;
47             end if;
48         end process reg;
49
50         data_out <= temp2;
51     end rtl;
52
```

accumulator8 Synthesize & RTL Schematic:

accumulator8

 

accumulator8

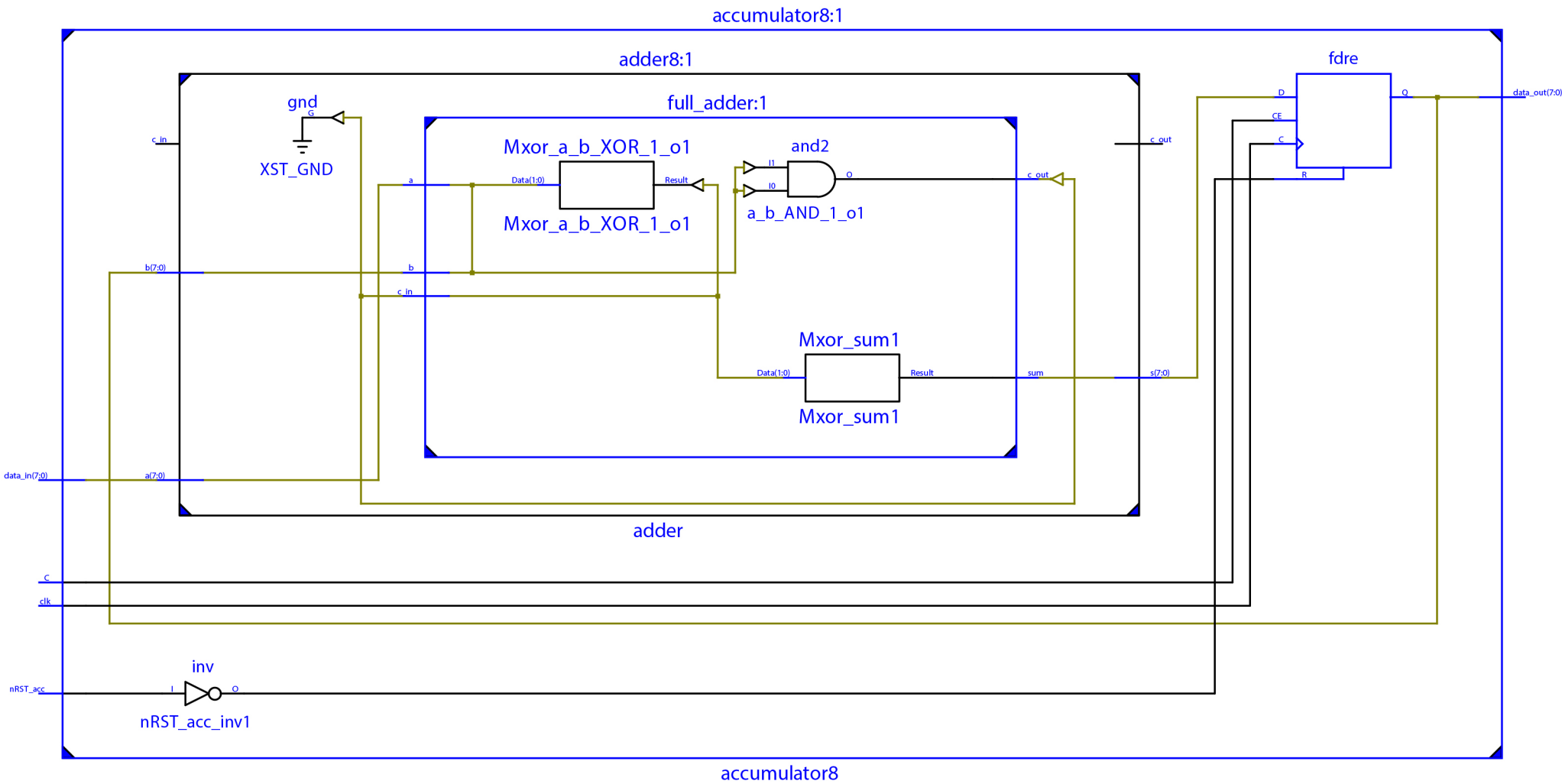

Adder8:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  vending_machine_processor
3  -- Module Name:   Adder8
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  ENTITY adder8 IS
9      PORT(
10         a : in std_logic_vector(7 downto 0);
11         b : in std_logic_vector(7 downto 0);
12         c_in: in std_logic;
13         s: out std_logic_vector(7 downto 0);
14         c_out: out std_logic);
15 end adder8;
16
17 architecture model of adder8 is
18     signal c: std_logic_vector(7 downto 1) := (others => '0');
19     COMPONENT full_adder
20         PORT(
21             a : IN STD_LOGIC;
22             b : IN STD_LOGIC;
23             c_in : IN STD_LOGIC;
24             sum : OUT STD_LOGIC;
25             c_out : OUT STD_LOGIC);
26     END COMPONENT;
27 BEGIN
28     bit0 : full_adder PORT MAP (a(0),b(0),c_in,s(0),c(1));
29     bit1 : full_adder PORT MAP (a(1),b(1),c(1),s(1),c(2));
30     bit2 : full_adder PORT MAP (a(2),b(2),c(2),s(2),c(3));
31     bit3 : full_adder PORT MAP (a(3),b(3),c(3),s(3),c(4));
32     bit4 : full_adder PORT MAP (a(4),b(4),c(4),s(4),c(5));
33     bit5 : full_adder PORT MAP (a(5),b(5),c(5),s(5),c(6));
34     bit6 : full_adder PORT MAP (a(6),b(6),c(6),s(6),c(7));
35     bit7 : full_adder PORT MAP (a(7),b(7),c(7),s(7),c_out);
36 END model;
```



full_Adder:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  vending_machine_processor
3  -- Module Name:   full_adder
4  LIBRARY ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  ENTITY full_adder IS
9      PORT(
10         a : IN STD_LOGIC;
11         b : IN STD_LOGIC;
12         c_in : IN STD_LOGIC;
13         sum : OUT STD_LOGIC;
14         c_out : OUT STD_LOGIC);
15 END full_adder;
16
17 ARCHITECTURE model OF full_adder IS
18 BEGIN
19     sum <= a XOR b XOR c_in;
20     c_out <= (a AND b) OR (c_in AND (a XOR b));
21 END model;
```


Comparator8:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name: vending_machine_processor
3  -- Module Name: comparator8- structural
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity comparator8 is
9      port(
10         a : in std_logic_vector(7 downto 0);
11         b : in std_logic_vector(7 downto 0);
12         g_out : out std_logic;
13         e_out : out std_logic;
14         l_out : out std_logic);
15 end comparator8;
16
17 architecture structural of comparator8 is
18     signal g : std_logic_vector(7 downto 0);
19     signal e : std_logic_vector(7 downto 0);
20     signal l : std_logic_vector(7 downto 0);
21
22     component comparator_1bit
23     port(
24         a : in std_logic;
25         b : in std_logic;
26         g : out std_logic;
27         e : out std_logic;
28         l : out std_logic);
29 end component;
30
31     component comparator_CO --comparator_consider_order
32     port(
33         g_old : in std_logic;
34         e_old : in std_logic;
35         l_old : in std_logic;
36         a : in std_logic;
37         b : in std_logic;
38         g : out std_logic;
39         e : out std_logic;
40         l : out std_logic);
41 end component;
42
43 begin
44     bit7 : comparator_1bit port map (a(7), b(7), g(6), e(6), l(6));
45     bit6 : comparator_CO port map (g(6), e(6), l(6), a(6), b(6), g(5), e(5), l(5));
46     bit5 : comparator_CO port map (g(5), e(5), l(5), a(5), b(5), g(4), e(4), l(4));
47     bit4 : comparator_CO port map (g(4), e(4), l(4), a(4), b(4), g(3), e(3), l(3));
48     bit3 : comparator_CO port map (g(3), e(3), l(3), a(3), b(3), g(2), e(2), l(2));
49     bit2 : comparator_CO port map (g(2), e(2), l(2), a(2), b(2), g(1), e(1), l(1));
50     bit1 : comparator_CO port map (g(1), e(1), l(1), a(1), b(1), g(0), e(0), l(0));
51     bit0 : comparator_CO port map (g(0), e(0), l(0), a(0), b(0), g_out, e_out, l_out);
52
53 end structural;
```

Comparator8 Synthesize & RTL Schematic:

  

Comparator C

comparator_consider_order

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  vending_machine_processor
3  -- Module Name:   comparator_CO: comparator_consider_order - structural
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity comparator_CO is --comparator_consider_order
9      port(
10         g_old : in std_logic;
11         e_old : in std_logic;
12         l_old : in std_logic;
13         a : in std_logic;
14         b : in std_logic;
15         g : out std_logic;
16         e : out std_logic;
17         l : out std_logic);
18 end comparator_CO;
19
20 architecture structural of comparator_CO is
21 begin
22     g <= (a and (not b) and e_old) or g_old;
23     e <= (a xnor b) and e_old;
24     l <= ((not a) and b and e_old) or l_old;
25 end structural ;
26
```

Comparator t:

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  vending_machine_processor
3  -- Module Name:   comparator_1bit- structural
4  library ieee;
5  use ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity comparator_1bit is
9      port(
10         a : in std_logic;
11         b : in std_logic;
12         g : out std_logic;
13         e : out std_logic;
14         l : out std_logic);
15 end comparator_1bit;
16
17 architecture structural of comparator_1bit is
18 begin
19     g <= (a and (not b));
20     e <= (a xnor b);
21     l <= ((not a) and b);
22 end structural;
23
```

subtractor8

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  vending_machine_processor
3  -- Module Name:  subtractor8 - structural
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity subtractor8 is
9      port(
10         a : in std_logic_vector(7 downto 0);
11         b : in std_logic_vector(7 downto 0);
12         result : out std_logic_vector(7 downto 0)
13     );
14 end subtractor8;
15
16 architecture structural of subtractor8 is
17     component adder8 IS
18     port(
19         a : in std_logic_vector(7 downto 0);
20         b : in std_logic_vector(7 downto 0);
21         c_in: in std_logic;
22         s: out std_logic_vector(7 downto 0);
23         c_out: out std_logic
24     );
25 end component;
26
27 signal c_in : std_logic;
28 signal c_out : std_logic;
29 signal not_b : std_logic_vector(7 downto 0);
30
31 begin
32     not_b <= (not b);
33     c_in <= '1';
34     subtractor : adder8 port map (a, not_b, c_in, result, c_out);
35 end structural;
36
```

mux21

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name: vending_machine_processor
3  -- Module Name: mux21
4  library ieee;
5  USE ieee.std_logic_1164.all;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity mux21 is
9      port(
10         A : in std_logic_vector(7 downto 0);
11         B : in std_logic_vector(7 downto 0);
12         s : in std_logic;
13         output : out std_logic_vector(7 downto 0)
14     );
15 end mux21;
16
17 architecture model of mux21 is
18 begin
19     output <= A when (s = '0') else
20             B when (s = '1');
21 end model;
```

Reference:

https://github.com/MohammadNiknam17/vending_machine_processor